

Bipolar Voltage Outputs for the TLV56xx Family of DACs

Frank Schoofs

Analog and Mixed Signal Solutions

ABSTRACT

A method for generating a symmetrical, bipolar, output swing voltage from a TI TLV56xx-family digital-to-analog converter (DAC) by using a bipolar operational amplifier (op amp), TLE2142, is presented. The resulting output voltage has a wide range that is limited only by the choice of op amp used for conditioning the DAC output signal. The example in this report realizes an output voltage range of ± 13.8 V for a 10-k Ω load.

Design Problem

Some applications require digital-to-analog signal conversion with a bipolar output-voltage range. The output-voltage range of a standard unipolar DAC is generally between zero and $2 \times V_{ref}$, however, it can easily be signal-conditioned to produce a bipolar range.

Solution

The DAC's output voltage is

$$OUT = 2 V_{ref} \frac{CODE}{(0 \times 1000)}$$

where *CODE* is the DAC's digital input, *OUT* is its analog output, and V_{ref} is the reference voltage, which may be already integrated into the DAC. Within the 12-bit TLV56xx family of DACs, *CODE* can have any value between 0x000 and 0xFF F.

The conversion of a strictly non-negative voltage range into a symmetrical bipolar range is achieved using a standard op amp connected as a difference amplifier as shown in Figure 1.

Referring to Figure 1, the output voltage of the op amp A_1 is

$$V_O = \frac{R_4}{R_3 + R_4} \left(1 + \frac{R_2}{R_1} \right) OUT - \frac{R_2}{R_1} V_{ref} \quad (1)$$

When $R_2/R_1 = R_4/R_3$ the op amp works as a real differential amplifier and, in this case, equation (1) simplifies to:

$$V_O = \frac{R_2}{R_1} (OUT - V_{ref}) = A_{DM} (OUT - V_{ref})$$

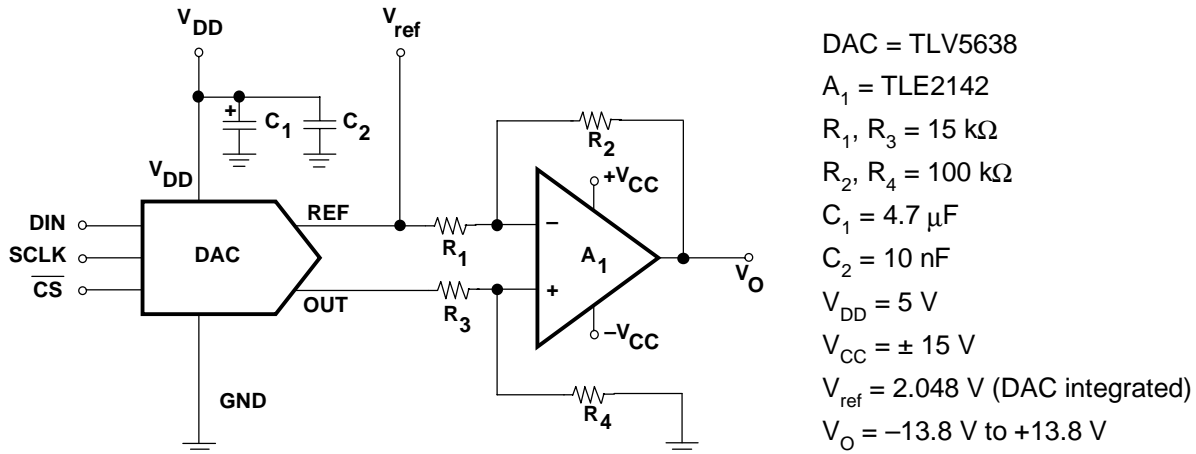


Figure 1. TLV56xx With Bipolar Output

$$\frac{R_4}{R_3} = (1+x) \frac{R_2}{R_1}; \quad |x| \ll 1$$

In this case, equation (1) becomes

$$V_O = \frac{R_2}{R_1} \left[\frac{\left(1 + \frac{R_2}{R_1}\right)(1+x)}{1 + \frac{R_2}{R_1}(1+x)} OUT - V_{ref} \right] \approx A_{DM} \left[(OUT - V_{ref}) + \frac{OUT}{1 + \frac{R_2}{R_1}} x + O(x^2) \right]$$

When *OUT* and *V_{ref}* share the common-mode voltage, *V_{CM}*, the output voltage and the common-mode gain are nonzero and

$$A_{CM} = \frac{V_O}{V_{CM}} \approx \left(\frac{R_2}{R_1 + R_2} \right) x$$

The common-mode rejection ratio, *CMRR*, is then

$$CMRR = \left| \frac{A_{DM}}{A_{CM}} \right| = \left(\frac{R_1 + R_2}{R_1} \right) \frac{1}{|x|} \approx \frac{R_2}{R_1} \cdot \frac{1}{|x|}; \quad R_2 \gg R_1$$

This result shows that it is crucial to choose very precise pairs of resistors to obtain an acceptably-high value of the common-mode rejection ratio.

Conclusion

An easy, cost-effective method to generate bipolar outputs from a DAC is by using a bipolar difference amplifier to condition the DAC's output signal. The output voltage range depends mainly on the choice of op amp and its resistors. However, an acceptable common-mode rejection ratio can be obtained only by using resistor pairs of very high accuracy. Therefore, for those applications that are *CMRR* critical, an instrumental amplifier should be used instead.

IMPORTANT NOTICE

Texas Instruments and its subsidiaries (TI) reserve the right to make changes to their products or to discontinue any product or service without notice, and advise customers to obtain the latest version of relevant information to verify, before placing orders, that information being relied on is current and complete. All products are sold subject to the terms and conditions of sale supplied at the time of order acknowledgment, including those pertaining to warranty, patent infringement, and limitation of liability.

TI warrants performance of its semiconductor products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are utilized to the extent TI deems necessary to support this warranty. Specific testing of all parameters of each device is not necessarily performed, except those mandated by government requirements.

Customers are responsible for their applications using TI components.

In order to minimize risks associated with the customer's applications, adequate design and operating safeguards must be provided by the customer to minimize inherent or procedural hazards.

TI assumes no liability for applications assistance or customer product design. TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right of TI covering or relating to any combination, machine, or process in which such semiconductor products or services might be or are used. TI's publication of information regarding any third party's products or services does not constitute TI's approval, warranty or endorsement thereof.